



M.C. Smith


Adapted from:

“VHDL Quick Start” by Peter J. Ashenden

VHDL INTRO (PART II)

VHDL Code Example
 
```
LIBRARY ieee;
USE ieee.std_logic_1164.ALL;
ENTITY example1 IS
    PORT (x1,x2,x3 : IN std_logic;
          f          : OUT std_logic);
END example1;
ARCHITECTURE LogicFunc OF example1 IS
BEGIN
    f <= (x1 AND x2) OR (NOT x2 AND x3);
END LogicFunc;
```



Boolean Operators In VHDL

- VHDL has built-in support for the following operators
 - AND logical AND
 - OR logical OR
 - NOT logical NOT
 - NAND, NOR, XOR, XNOR
- Assignment operator: `<=`
 - A variable (usually an output, mode **OUT**) should be assigned the result of the logic expression on the right hand side of the operator
- VHDL does not assume any precedence of logic operators... Use parentheses in expressions to determine precedence
 - Exception to this is NOT logical operator
- In VHDL, a logic expression is called a ***simple assignment statement***. There are other types that will be introduced that are useful for more complex circuits

Native Operators



- Logical - defined for type bit, bit_vector, boolean*

- AND, NAND
- OR, NOR
- XOR, XNOR
- NOT

*•The NOT operator has highest precedence
•The rest are (and, nand, xor, etc.) are of equal precedence so you just used parentheses where necessary*

- Relational - defined for types bit, bit_vector, integer*

- = (equal to)
- /= (not equal to)
- < (less than)
- <= (less than or equal to)
- > (greater than)
- >= (greater than or equal to)

*•Relational operators return a boolean value
•When comparing vectors of different lengths, the comparison is done from left to right. Therefore "111" is greater than "10111"*

** overloaded for std_logic, std_logic_vector; will explain this shortly...*

Native Operators (contd.)

- Unary Arithmetic - defined for type integer*
 - - (arithmetic negate)
- Arithmetic - defined for type integer*
 - +(addition), *(multiplication)
 - - (subtraction)
 - /, mod, rem, abs, **
- Concatenation - defined for strings
 - &
- Note, a STRING is any sequence of characters, therefore a std_logic_vector is an example of a STRING

VERY
IMPORTANT!!!!

** overloaded for std_logic, std_logic_vector; will explain this shortly...*

Overloaded Operators



- In VHDL, the scope of all of the previous operators can be extended (or overloaded) to accept any type supported by the language, e.g.,
 - assume a declaration of a 16-bit vector as
SIGNAL pc IS std_logic_vector(15 DOWNT0 0);
 - then a valid signal assignment is
pc <= pc + 3;
 - assuming the '+' operator has been overloaded to
 - accept std_logic_vector and integer operands
- The std_logic_1164 package defines overloaded logical operators (AND, OR, NOT, etc.,) for the std_logic and std_logic_vector types

Legal VHDL Identifiers



- Letters, digits, and underscores only (first character must be a letter)
- The last character cannot be an underscore
- Two underscores in succession are not allowed
- Using reserved words is not allowed (the VHDL editor will highlight reserved words for this reason)
- Examples
 - Legal
 - tx_clk, Three_State_Enable, sel7D, HIT_1124
 - Not Legal
 - _tx_clk, 8B10B, large#num, case, clk_

Operators Summary



- Logical
 - and, or, nand, nor, xor, xnor, not
 - NOTE: nand and nor not associative
- Relational
 - =, /=, <, <=, >, >=
- Shift
 - sll, srl, sla, sra, rol, ror
 - Shift logical or arithmetic
 - Rotate left/right
- Adding
 - +, -, &
- Multiplying
 - *, /, mod, rem
 - $a \text{ rem } b = a - (a/b) * b$
 - $a \text{ mod } b = a - b * n$ (for some n)
- Other
 - abs, **

VHDL Assignment Stmts



- VHDL provides several types of statements that can be used to assign logic values to signals
 - Simple assignment statements
 - Used previously, for logic or arithmetic expressions
 - Selected signal assignments
 - Conditional signal assignments
 - Generate statements
 - If then else statements
 - If-then-- Case statements

Architecture Body May Contain:

- Concurrent Signal Assignment statements (CSAs)
 - $a \leq b + c;$
 - Activated when any of the associated signals change their values
 - Independent from other statements in the given architecture
- Component Instantiations
 - Pairs the entity with the architecture
 - Defines a sub-component of the design
 - Associates signals or values with the ports
- Processes with behavioral descriptions
 - An independent sequential process representing the behavior of some portion of the design

CSAs Example

- Example below specifies a half adder
- Whenever A or B changes in value, both signal assignments will be activated concurrently → Hardware parallelism!

```
architecture dataflow of HalfAdder is  
begin
```

```
    Sum <= A xor B;
```

```
    Carry <= A and B;
```

```
end architecture;
```

Component Instantiation

- Introduces a relationship to a component declaration
- Port map may be either *named* or *positional*
- Either way, it must match!

```
reg5 : fill_reg  
port map ( clk => clk,  
           rst => rst,  
           write => write_comp,  
           read => readout,  
           data_in => dataout_comp,  
           FFout => FFout,  
           data_out => datareg5_out);
```

Preferred!

```
reg5 : fill_reg  
port map (clk, rst, write_comp,  
           readout, dataout_comp,  
           FFout, datareg5_out);
```

Other Assignment Statements



- For ***concurrent assignment statements (or concurrent signal assignments - CSAs)*** the order in which they appear in VHDL code does not affect the meaning of the code
- VHDL provides a second category of statements, ***sequential assignment statements***, for which the ordering of the statements may affect the meaning of the code
 - If **then else** and **case** statements are examples of sequential stmts
- VHDL requires that sequential assignment statements be placed inside another statement, the ***process*** statement
- Therefore, all behavioral designs require caution!

What is a VHDL “Process” ?

- Processes are either awake or asleep (active or inactive)
- A process normally has a sensitivity list
 - When a signal in that sensitivity list changes value, the process wakes up and all of the sequential statements are “executed”
 - For example, a process with a clock signal in its sensitivity list will become active on changes of the clock signal
- At the end of the process, all outputs are assigned and the process goes back to sleep until the next time a signal changes in the sensitivity list

```
<label> process ( <sensitivity list> )  
    < process declarations >  
begin  
    < statements >  
end process <label>;
```

Process Statement

- Process executes or is evaluated whenever an event occurs on a signal in the sensitivity list
 - Remember: No sensitivity list is required, BUT if not, wait statements must be used in the process
- Multiple processes can execute concurrently
- The statements describing the behavior are executed **sequentially**
 - This is true from a simulation standpoint
 - From a synthesized hardware point-of-view, multiple assignments to a single signal (variable) generally implies multiplexing of the assignments to produce a single output
- Assignments made inside the process are not visible outside the process until all statements in the process have been evaluated
 - If there are multiple assignments to the same signal inside a process, only the last one has any visible effect
- The <label> is optional

Process Example (from a simulation)

```
process
begin
  wait for 15 ns;
  clk <= not(clk);
end process;
```

```
process (clk, rst)
begin
  if rst = '1' then
    readout <= '0';
  elsif (clk' event and clk = '1') then
    if (fout = '1') then
      readout <= '1';
    else
      readout <= '0';
    end if;
  end if;
end process;
```

```
<label> process ( <sensitivity list> )
  < process declarations >
begin
  < statements >
end process <label>;
```

*2 processes operating
in parallel*

1st process generates the clock

*2nd process has the clock in the
sensitivity list*

Behavioral Statements



- Wait Statement – causes suspension of a process or procedure
 - WAIT ON <sensitivity> UNTIL <expression> FOR <time>
- Examples:
 - WAIT ON A, B, C;
 - WAIT UNTIL A > 10;
 - WAIT FOR 30ns;
 - WAIT ON A FOR 100ns;
 - WAIT UNTIL C < 4 FOR 50ms;
 - WAIT ON B UNTIL A > 4;
 - WAIT ON C UNTIL B > 5 FOR 30us;
 - WAIT; -- suspends forever

Concurrency

- “Concurrent” means **nonprocedural (i.e. not in a Process statement!)**
 - The order in which the CSA stmts appear textually has nothing to do with the order in which they execute
 - They execute at the same time!!!!!!!!!!
- Note: INT1 and INT2 are internal signals, used only within the **architecture** (keep scope in mind)

```
entity XOR2_OP is  
port (A, B : in BIT;  
      Z : out BIT);  
end XOR2_OP;  
architecture AND_OR_CONCURRENT  
  of XOR2_OP is  
    signal INT1, INT2 : BIT;  
begin  
  INT1 <= A and not B;  
  INT2 <= not A and B;  
  Z <= INT1 or INT2;  
end AND_OR_CONCURRENT;
```


Concurrency (cont.)




- Concurrency is fundamental to hardware and VHDL!
- Think in terms of *parallel signal transformations*
- Design tips:
 - Large procedural descriptions are ***hard to synthesize***
 - Concurrency – must think about how it is ***realized*** – “visualize the possible hardware”
 - Think about design ***decomposition*** (modular and hierarchical)

- Next example shows two designs for an odd parity detector
- Think about which one will have better performance (i.e. yield a faster design)?

VHDL Stmts & Hardware Concurrency

 
 
```
entity OPARITY_DETECT is
port (A3,A2,A1,A0: in std_logic;
       OPARITY : out std_logic);
end OPARITY_DETECT;
architecture design1 of
    OPARITY_DETECT is
    signal INT1, INT2 : BIT;
begin
    INT1 <= A3 xor A2;
    INT2 <= INT1 xor A1;
    OPARITY <= INT2 xor A0;
end design1;
```



```
entity OPARITY_DETECT is
port (A3,A2,A1,A0: in std_logic;
       OPARITY : out std_logic);
end OPARITY_DETECT;
architecture design2 of
    OPARITY_DETECT is
    signal INT1, INT2 : BIT;
begin
    INT1 <= A3 xor A2;
    INT2 <= A0 xor A1;
    OPARITY <= INT2 xor INT1;
end design2;
```

Combinational Logic


- Can be described with concurrent statements
 - boolean equations
 - when-else
 - with-select-when
 - component instantiations
- Can be described with sequential statements
 - if-then-else
 - case-when

*Lets look at examples
of each...*

Combinational Logic w/ Boolean Equations

- Boolean Equations can be used in both concurrent and sequential signal assignment statements...
- A 4-1 multiplexer is shown below

 $x \leq (a \text{ AND NOT}(s(1)) \text{ AND NOT}(s(0))) \text{ OR}$
 $(b \text{ AND NOT}(s(1)) \text{ AND } s(0)) \text{ OR}$
 $(c \text{ AND } s(1) \text{ AND NOT}(s(0))) \text{ OR}$
 $(d \text{ AND } s(1) \text{ AND } s(0)) ;$



concurrent

Selective Signal Assignment: with-select-when



- Assignment based on a selection signal
- WHEN clauses must be mutually exclusive
- Use a WHEN OTHERS when all conditions are not specified
- Only one reference to the signal, only one assignment operator (<=)

WITH selection_signal SELECT

signal_name <= value_1 WHEN value_1 of selection_signal,

value_2 WHEN value_2 of selection_signal,

...

value_n WHEN value_n of selection_signal,

value_x WHEN OTHERS;


concurrent

Combinational Logic w/ Selective Signal Assignment

- The same 4-1 multiplexer is shown below

with s select

 $x \leq a$ when “00” ,
 b when “01” ,
 c when “10” ,
 d when others ;




concurrent

More on with-select-when

- You can use a range of values

```
with int_value select  
  x <= a when 0 to 3,  
    b when 4 | 6 | 8 ,  
    c when 10 ,  
    d when others ;
```

 

concurrent

Conditional Signal Assignment: when-else



- Assign a value based on conditions
- Any simple expression can be a condition
- Priority goes in order of appearance
- Only one reference to the signal, only one assignment operator (<=)
- Use a final ELSE to avoid latches


```
signal_name <= value_1 WHEN condition1 ELSE  
           value_2 WHEN condition2 ELSE  
           ...  
           value_n WHEN condition N ELSE  
           value_x ;
```

concurrent

Combinational Logic w/ Conditional Signal Assignment

- The same 4-1 multiplexer is shown below

 $x \leq a$ when ($s = "00"$) else
 b when ($s = "01"$) else
 c when ($s = "10"$) else
 d ;



concurrent

Combinational Logic w/ Conditional Signal Assignment



- The when conditions do not have to be mutually exclusive (as in with-select-when)
- A priority encoder is shown below
 - Order of the conditions matters!!!!!!

```
j <= w when (a = '1' ) else  
  x when (b = '1' ) else  
  y when (c = '1' ) else  
  z when (d = '1' ) else  
  "000" ;
```

concurrent

Combinatorial Logic w/ Sequential Statements



- Grouped inside **Process Statements**
- Processes are concurrent with *one another* and with *concurrent signal assignment statements*
- Order of sequential statements **does** make a difference in synthesis

sequential

Sequential Statements: if-then-else



- Used to select a set of statements to be executed
- Selection based on a boolean evaluation of a condition or set of conditions
- Absence of ELSE results in implicit memory (FF or latch)

IF condition(s) THEN

do something;

ELSIF condition_2 THEN -- optional

do something different;

ELSE -- optional

do something completely different;


END IF ;

sequential

if-then-else

 - 4-1 mux shown below

```
mux4_1: process (a, b, c, d, s)
begin
  if s = "00" then x <= a ;
    elsif s = "01" then x <= b ;
    elsif s = "10" then x <= c ;
    else x <= d ;
  end if;
end process mux4_1 ;
```



sequential

Sequential Statements: Case-When




```
CASE selection_signal IS
  WHEN value_1_of_selection_signal =>
    (do something) -- set of statements 1
  WHEN value_2_of_selection_signal =>
    (do something) -- set of statements 2
  ...
  WHEN value_N_of_selection_signal =>
    (do something) -- set of statements N
  WHEN OTHERS =>
    (do something) -- default action
END CASE ;
```

(sort of the sequential counterpart to the with-select-when)

sequential

The CASE Statement: 4-1 Mux
 
```
ARCHITECTURE archdesign OF design IS
  SIGNAL s: std_logic_vector(0 TO 1);
BEGIN
  mux4_1: PROCESS (a,b,c,d,s)
  BEGIN
    CASE s IS
      WHEN "00"    => x <= a;
      WHEN "01"    => x <= b;
      WHEN "10"    => x <= c;
      WHEN OTHERS  => x <= d;
    END CASE;
  END PROCESS mux4_1;
END archdesign;
```





sequential

Signal Assignment in Processes

Which Circuit do you think is Correct?
  
```
ARCHITECTURE arch_reg OF reg IS
  SIGNAL b: std_logic
  reg2: PROCESS
  BEGIN
    WAIT UNTIL clock = '1';
    b <= a;  -- after the rising clock edge, a goes to b
    c <= b;  -- after the rising clock edge, b goes to c
  END PROCESS reg2;
END arch_reg
```



Signal Assignment in Processes



- Inside processes, signals are not updated immediately
→ Instead, they are scheduled to be updated
- Signals are updated at the END PROCESS
- Therefore, on the previous slide, two registers will be synthesized ($c \leq b$ will be the old b)
- In some cases, the use of a concurrent statement outside the process will fix the problem, but this is not always possible
- So how else can we fix this problem ?

Variables

- When a concurrent signal assignment outside the process cannot be used, the previous problem can be avoided using a variable
 - Variables are like signals, BUT they can only be used inside a given PROCESS (signals are inside the architecture)
 - They cannot be used to communicate information between processes
 - Variables can be of any valid VHDL data type
 - The value assigned to a variable is available immediately
 - Assignment of variables is done using a colon (:), like this:
c := a AND b;

Using Variables vs. Signals



- Solution using a variable within a process:

-- assume a and c are signals defined elsewhere

ARCHITECTURE arch_reg **OF** reg **IS**

PROCESS

VARIABLE b: std_logic ;

BEGIN

WAIT UNTIL clock = '1' ;

 b := a ; *-- this is immediate*

 c <= b ; *-- this is scheduled*

END PROCESS ;


END arch_reg;

 Exercise #2: Architecture Declaration of a Comparator



- The entity declaration is as follows:

```
LIBRARY ieee;  
USE ieee.std_logic_1164.ALL;  
ENTITY compare IS PORT (  
    a, b    : IN std_logic_vector(3 DOWNTO 0);  
    a_eq_b : OUT std_logic);  
END compare;
```



- Write an architecture that causes **a_eq_b** to be asserted when **a** is equal to **b**
- Multiple solutions exist

Exercise #2: Three possible solutions



- Concurrent statement solution using a *conditional* assignment:

```
ARCHITECTURE df1_compare OF compare IS  
BEGIN  
    a_eq_b <= '1' WHEN a = b ELSE '0';  
END df1_compare;
```


- Concurrent statement solution using boolean equations:

```
ARCHITECTURE df2_compare OF compare IS  
BEGIN  
    a_eq_b <= NOT(  
        (a(0) XOR b(0)) OR  
        (a(1) XOR b(1)) OR  
        (a(2) XOR b(2)) OR  
        (a(3) XOR b(3)));  
END df2_compare;
```

 
Exercise #2: Three possible solutions

- Solution using a process with sequential statements:

```
ARCHITECTURE behv_compare OF compare IS  
BEGIN  
  comp: PROCESS (a, b)  
    BEGIN  
      IF a = b THEN  
        a_eq_b <= '1';  
      ELSE  
        a_eq_b <= '0';  
      END IF;  
    END PROCESS comp;  
END behv_compare;
```



Generate Statement



- Whenever we write structural VHDL code and instantiate components, we often create *instances* of a particular *component*
 - A multi-stage ripple carry adder made from a number of single-bit full adders might be an example
- If we need to create a large number of instances of a component, a more compact form is desired
- VHDL provides a feature called the **FOR GENERATE** statement
 - This statement provides a loop structure for describing regularly structured hierarchical code
 - **NOTE:** The loop cannot be terminated early

name : FOR N IN 1 TO 8 GENERATE

concurrent-statements

END GENERATE name;

Generate Statement Example

- In this example, we will build a 32-bit wide shift register using a DFF with clear

```
1 entity edge_triggered_Dff is
2     port (D: in bit; clk: in bit;
3           clr: in bit; en: in bit; Q: out bit);
4 end entity edge_triggered_Dff;
5 -----
6 architecture behavioral of edge_triggered_Dff is
7 begin
8     state_change: process(clk, clr) is
9     begin
10         if clr = '1' then
11             Q <= '0' after 2 ns;
12         elsif clk'event and clk = '1' and en = '1' then
13             Q <= D after 2 ns;
14         end if;
15     end process state_change;
16 end architecture behavioral;
```

Example Cont.

- Using this DFF, we want to place 32 of them in a row and wire the i^{th} input to the $(i-1)^{st}$ output
- The first input should be wired to *shift-in* and the last output should be wired to *shift-out*
- We could do this with 32 component instantiation statements of the form:

```
dff1: component edge_triggered_Dff
      port map (Sin, clk, clr, en, parallel_data(1) );
dff2: component edge_triggered_Dff
      port map (parallel_data(1), clk, clr, en, parallel_data(2) );
dff3: ...
```

Example Cont.

- Or... we could use *generate* to do the work for us

```
shift_reg: for i in 1 to 32 generate
begin
    dffx: generate
    begin
        dff: component edge_triggered_Dff
            port map (parallel_data(i-1), clk, clr, en, parallel_data(i) );
        end generate dffx;
    end generate shift_reg;
```

- Here, we are placing 32 copies of our DFF and wiring them up. There is a problem, however... There is no 0 element ($i-1$ when $i=1$)
- Another problem exists at the 32nd element where we need to wire the shift out

32-bit Shift Register

```
1 entity shift_right_32 is
2     port (Sin, clk, en, clr: in bit; Sout: out bit);
3 end entity shift_right_32;
4 -----
5 architecture reg32 of shift_right_32 is
6     signal parallel_data: bit_vector(1 to 32);
7
8     component edge_triggered_Dff
9         port (D: in bit; clk: in bit;
10             clr: in bit; en: in bit; Q: out bit);
11     end component edge_triggered_Dff;
12
13 begin
14     shift_reg: for i in 1 to 32 generate
15     begin
16         dff_left: if i = 1 generate
17         begin
18             dff: component edge_triggered_Dff
19                 port map (Sin, clk, clr, en, parallel_data(i) );
20             end generate dff_left;
21         dff_others: if ((i > 1) and (i < 32)) generate
22         begin
23             dff: component edge_triggered_Dff
24                 port map (parallel_data(i-1), clk, clr, en, parallel_data(i) );
25             end generate dff_others;
26         dff_right: if i = 32 generate
27         begin
28             dff: component edge_triggered_Dff
29                 port map (parallel_data(i-1), clk, clr, en, Sout);
30             end generate dff_right;
31         end generate shift_reg;
32 end architecture;
```

Architecture Example

Library IEEE;

```
use IEEE.STD_LOGIC_1164.all;  
use IEEE.STD_LOGIC_ARITH.all;  
use IEEE.STD_LOGIC_UNSIGNED.all;
```

entity count_example **is**

port(

```
clk : in std_logic;  
rst : in std_logic;  
enable : in std_logic;  
load : in std_logic;  
data_in : in std_logic_vector(4 downto 0);  
data_out: out std_logic_vector(4 downto 0));
```

```
end count_example;
```

Libraries

Architecture Example (cont.)



```
architecture version1 of count_example is  
  component adder  
    generic ( WIDTH : INTEGER := 8)  
    port (  
      in1 :in std_logic_vector(WIDTH-1 downto 0);  
      in2 :in std_logic_vector(WIDTH-1 downto 0);  
      out :out std_logic_vector(WIDTH-1 downto 0)  
    );  
  signal CNT :std_logic_vector(4 downto 0);  
  signal result :std_logic_vector(4 downto 0);  
  CONSTANT ONE :std_logic_vector(4 downto 0) := "00001";
```


Architecture Example (cont.)

```
begin
data_out <= CNT;
    adder1 : adder
        generic map ( WIDTH => 5)
        port map ( in1 => CNT,  in2 => ONE,    out => result );
process (clk, rst)
begin
if rst = ' 1' then
    CNT <= "00000";
elsif (clk' event and clk = ' 1' ) then
    if (load = ' 1' ) then
        CNT <= data_in;
    elsif (enable = ' 1' ) then
        CNT <= result;
    else
        CNT <= CNT;
    end if;
end if;
end if;
end process;
end version1;
```

Will this code synthesize?



```
entity my_code is
    port(A,B,CLK: in std_logic;
          D: out std_logic);
end my_code;
architecture my_arch of my_code is
    signal C: std_logic;
begin
    process(CLK)
    begin
        if (CLK='1' and CLK'event) then
            C <= A and B;
        end if;
    end process;
end my_arch;
```